



**WEST BENGAL STATE UNIVERSITY**  
B.Sc. Honours/Programme 2nd Semester Examination, 2022

**ELSHGEC02T/ELSGCOR02T-ELECTRONICS (GE2/DSC2)**

Time Allotted: 2 Hours

Full Marks: 40

*The figures in the margin indicate full marks.  
Candidates should answer in their own words and adhere to the word limit as practicable.  
All symbols are of usual significance.*

**GROUP-A**

1. Answer any *five* questions from the following: 2×5 = 10
- (a) What is virtual ground of an OP-Amp?
  - (b) What are the assumptions made from ideal OP-Amp characteristics?
  - (c) What is Karnaugh map?
  - (d) What do you mean by binary coded decimal (BCD)?
  - (e) Define positive and negative logic system.
  - (f) What is the significance of “Slew rate”?
  - (g) What is the Master-slave flip-flop? Why is it so called?
  - (h) The sum and the difference of two binary numbers are 1110 and 10 respectively. Find the two numbers.

**GROUP-B**

**Answer any six questions from the following** 5×6 = 30

2. (a) Define common mode gain of an OP-Amp. 2+3
- (b) Describe the principle of an OP-Amp non-inverting adder with circuit diagram.
3. (a) State De Morgan’s theorem. 2+3
- (b) Establish the following identities:
- (i)  $\overline{(\overline{A} + B)} + (\overline{A} + \overline{B}) = A$
  - (ii)  $\overline{AB} + \overline{A} + AB = 1$
  - (iii)  $A + AB = A$
4. Define a register. Construct a 4-bit shift register using D-type flip-flop. 1+4

5. (a) Define minterm and maxterm. 1+2+2  
 (b) Simplify the following function using Karnaugh map.  
 (i)  $F(ABCD) = \sum m(0, 2, 5, 7, 8, 10, 13, 15)$   
 (ii)  $F(ABCD) = \sum m(0, 1, 2, 5, 7, 8, 9, 10, 13, 15)$
6. Design a 4:1 multiplexer using logic gates and explain its operation by truth table.
7. (a) Convert  $(364.07)_8$  to decimal. 2+3  
 (b) Verify the Boolean identities.  

$$AB + \bar{A}C = (A + B)(\bar{C} + B)$$
8. (a) What is the function of the PRESET and CLEAR input of a flip-flop.  $1\frac{1}{2} + 1\frac{1}{2} + 2$   
 (b) Differentiate between asynchronous and synchronous counter.
9. (a) What is the difference between astable, monostable and bistable Multivibrator?  $2\frac{1}{2} + 2\frac{1}{2}$   
 (b) Draw the simplified internal circuit diagram of 555 timer IC.

**N.B. :** Students have to complete submission of their Answer Scripts through E-mail / Whatsapp to their own respective colleges on the same day / date of examination within 1 hour after end of exam. University / College authorities will not be held responsible for wrong submission (at in proper address). Students are strongly advised not to submit multiple copies of the same answer script.

—x—